
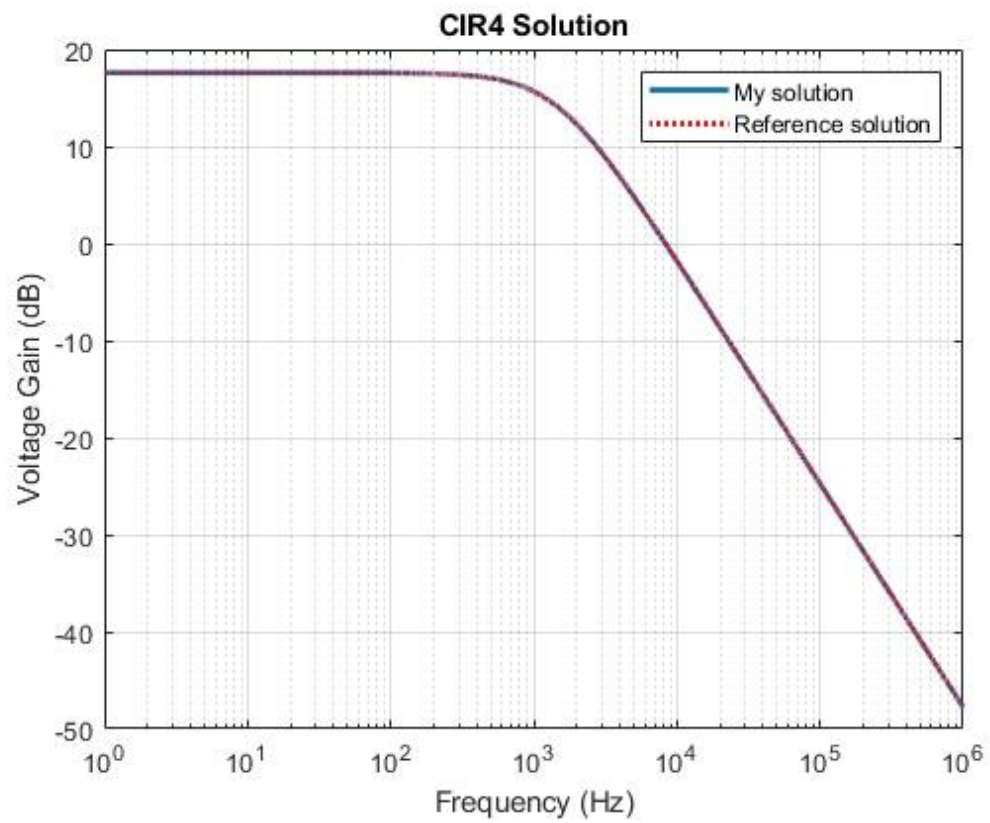



CIR4 filter Voltage Gain

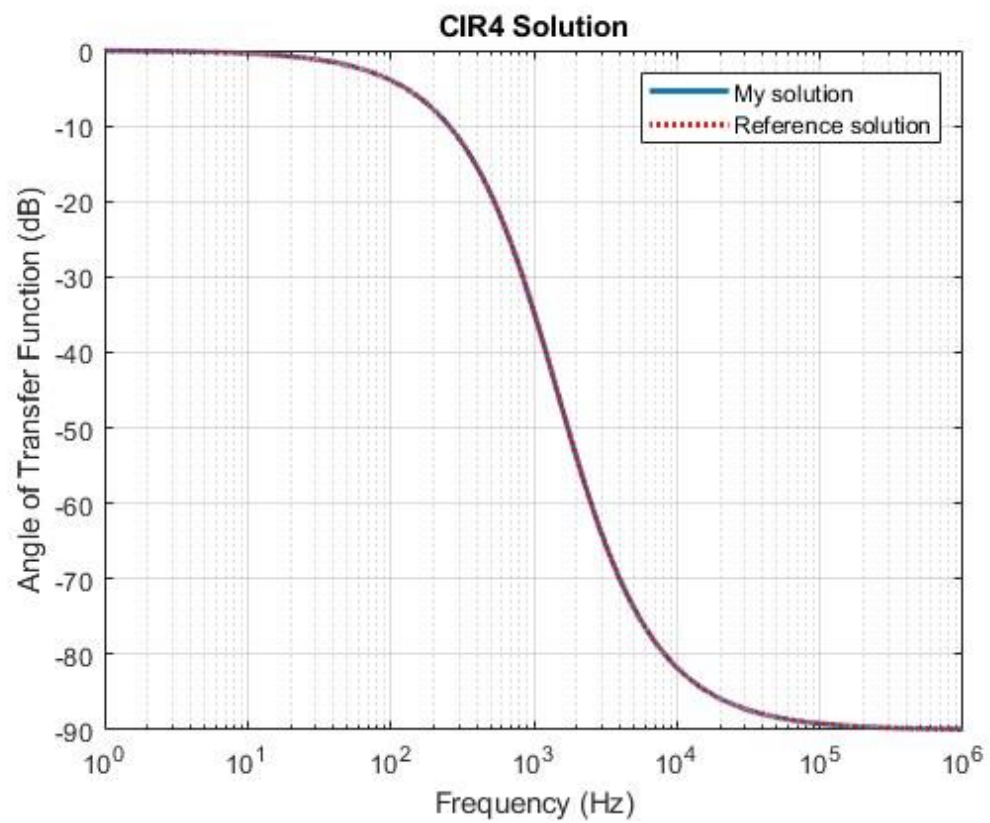


CIR4 filter Angle of Transfer Function




LC filter Voltage Gain

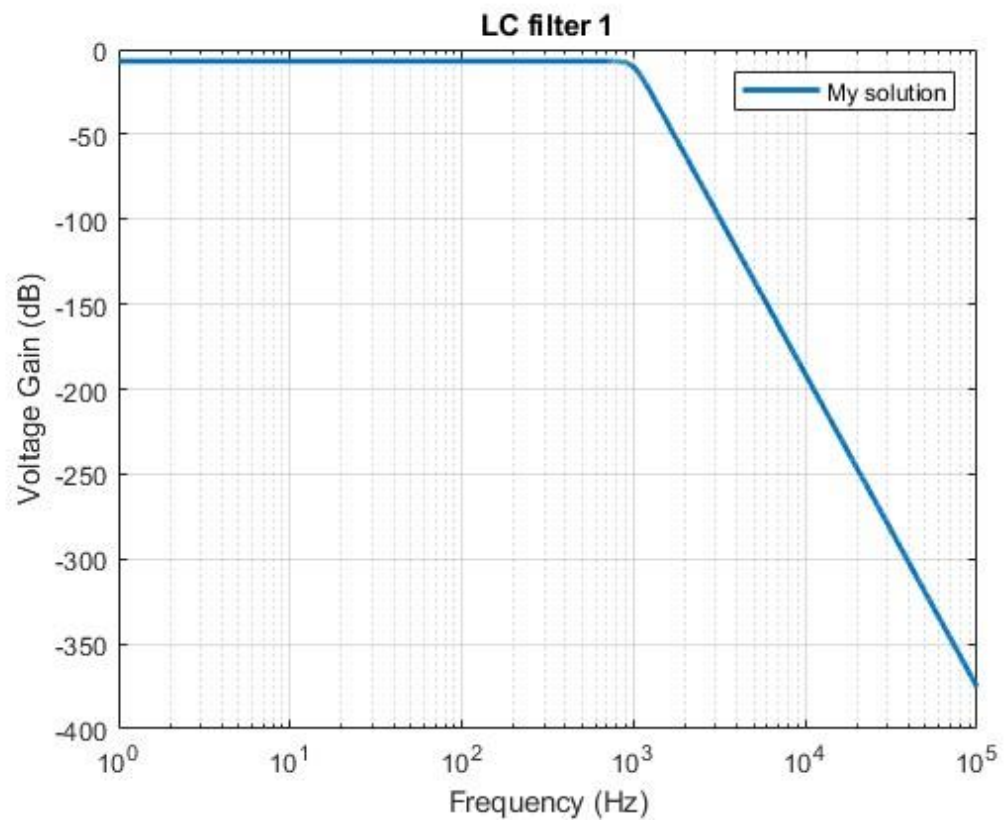


LC filter Angle of Transfer Function

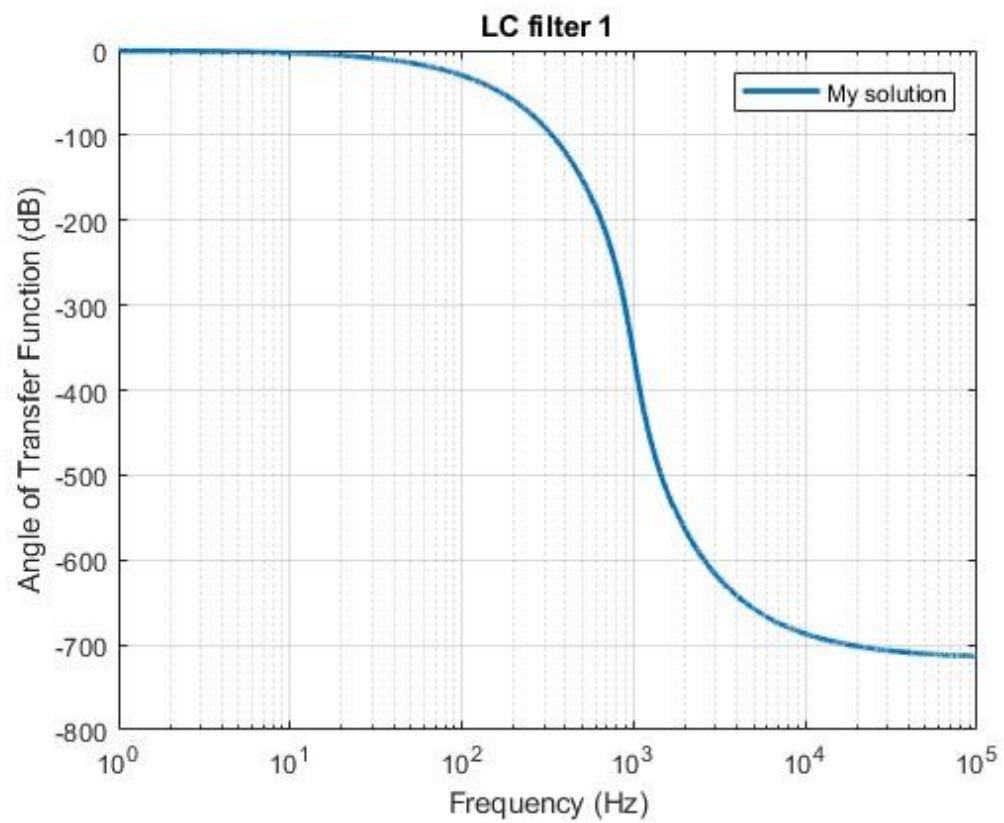


Chebyshev filter Voltage Gain

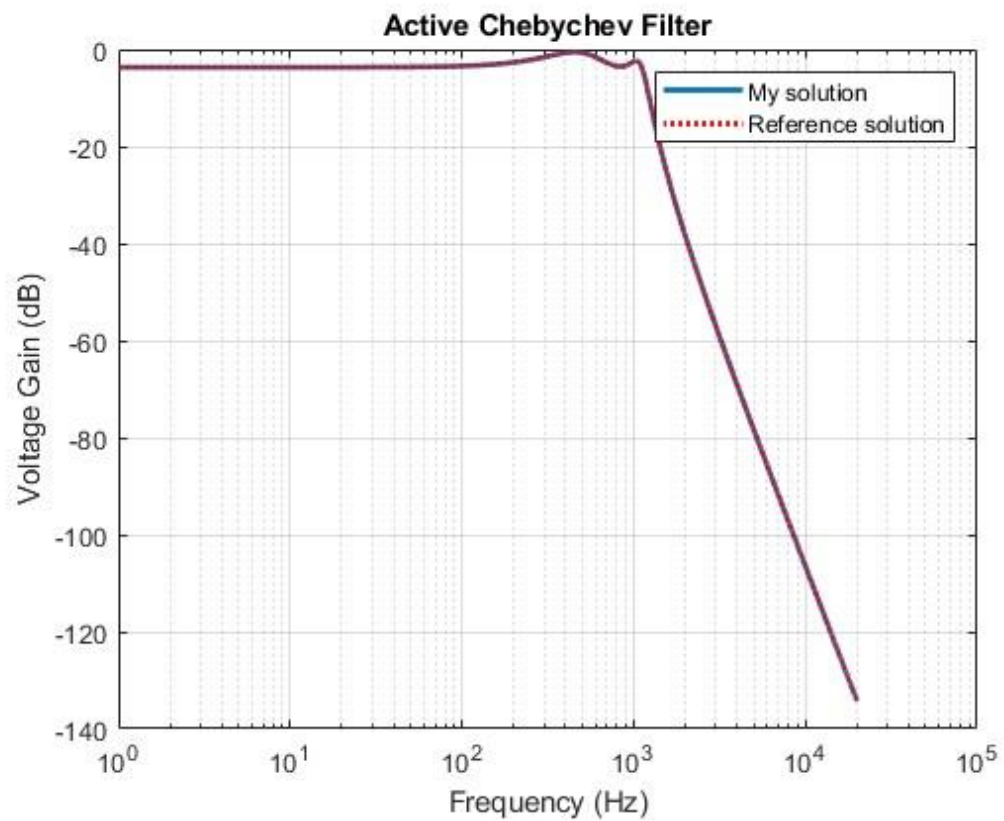

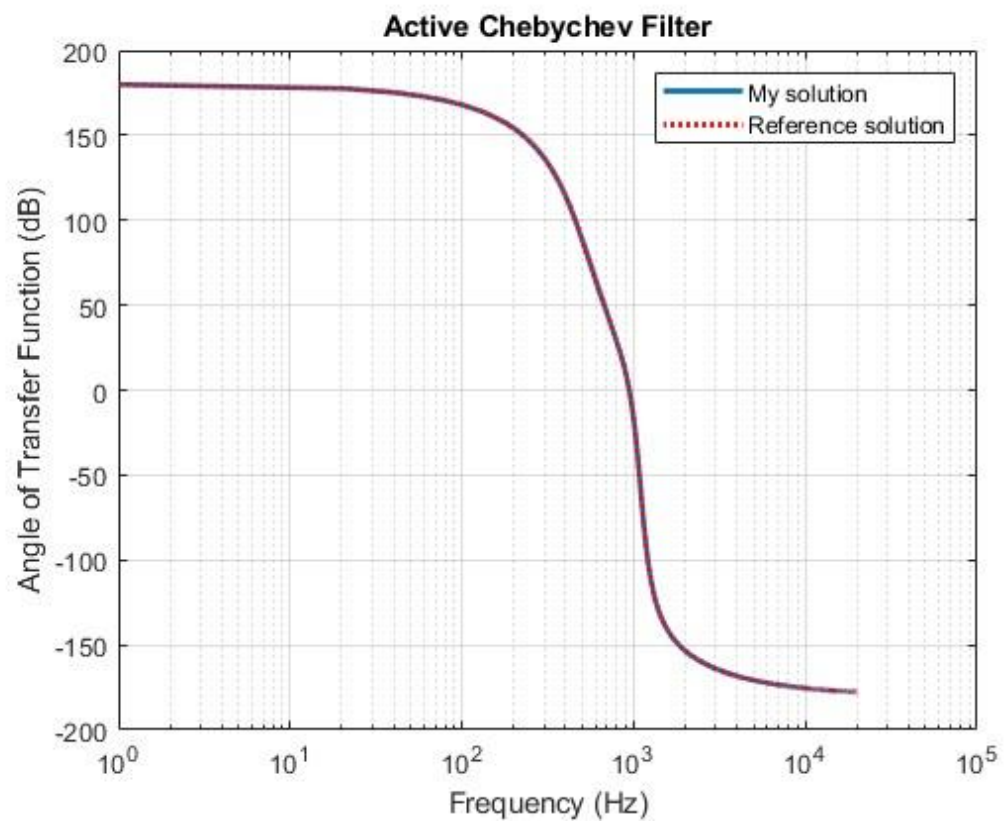Chebyshev filter Angle of Transfer Function



Chebyshev filter with Opamp Voltage Gain

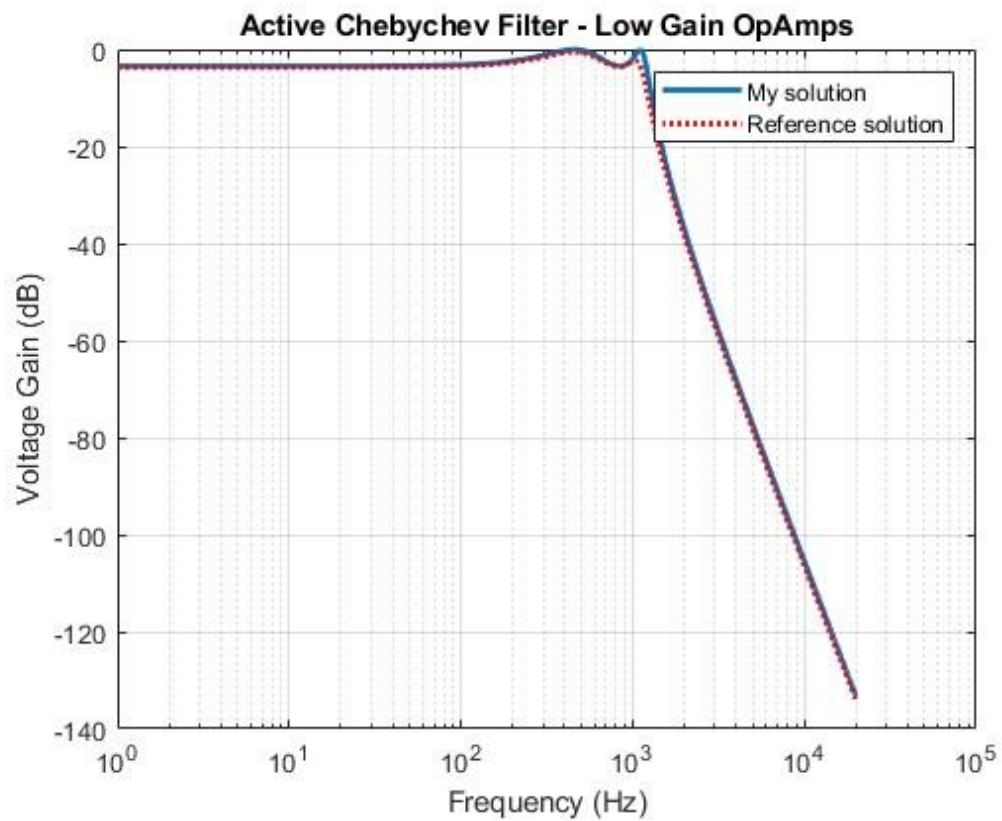

Chebyshev filter with Opamp Angle of Transfer Function

